

Introduction to VHDL

Professor Gregory Moss
Electrical & Computer Engineering Technology
Purdue University

VHDL

VHSIC Hardware Description Language
(Very High Speed Integrated Circuit)

IEEE Standard 1076-1993 (& others)

concurrent language \Rightarrow circuit description
documentation \rightarrow simulation \rightarrow synthesis


describes a model for a digital device

- gate \Leftrightarrow system
 - specify external view & internal view
- | | |
|--------------------|---------------------|
| ↓ | ↓ |
| interface | body |
| input/output ports | functionality |
| entity | architecture |

Entity & Architecture

INPUTS

OUTPUTS

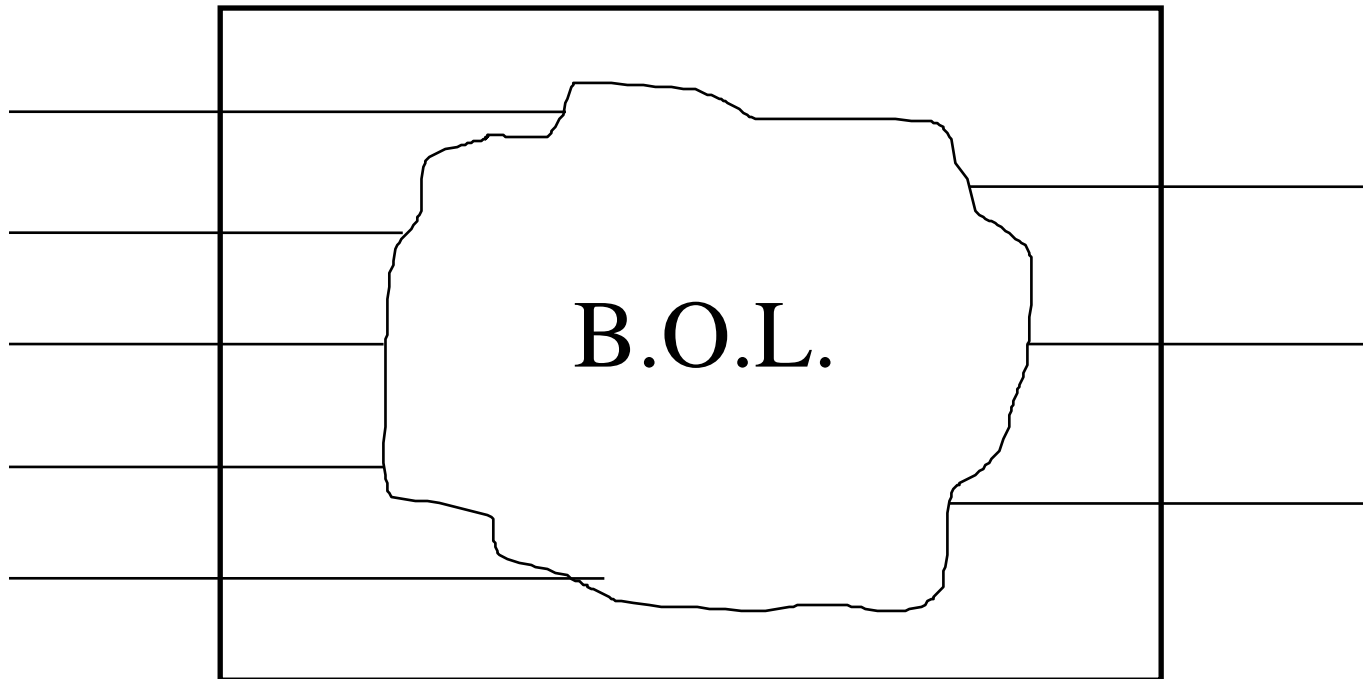

B.O.L. = "Blob Of Logic"

Basic VHDL building blocks

A VHDL design entity is a pairing of:


entity declaration

- describes the design I/O


architecture body

- describes the function of a design entity
- contains any combination of behavioral, structural, or dataflow descriptions

Entity

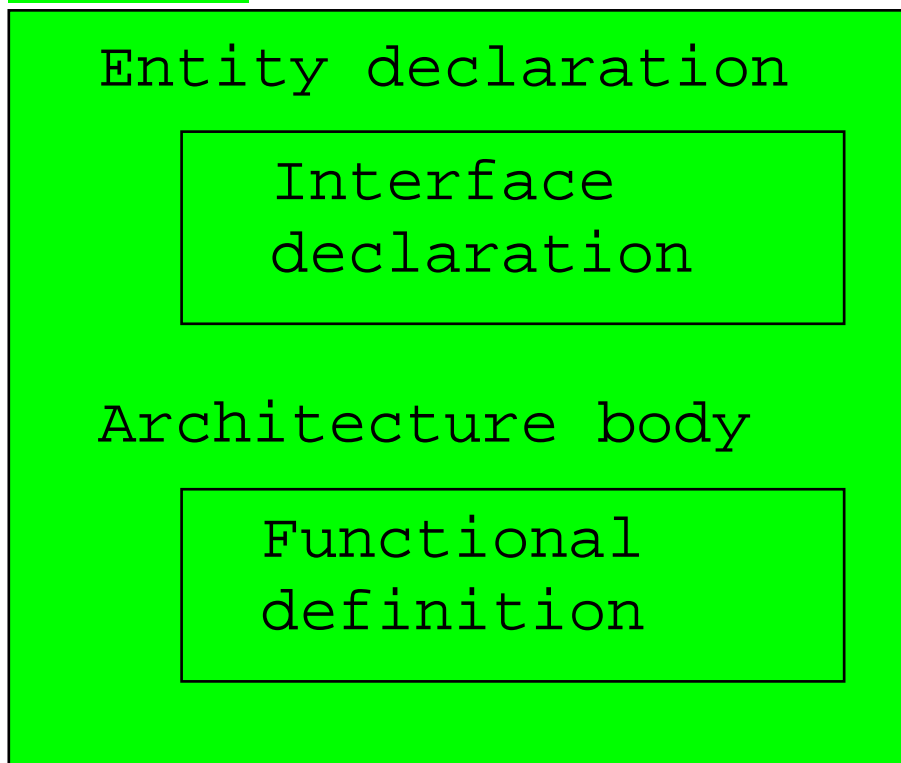


Entity Declaration

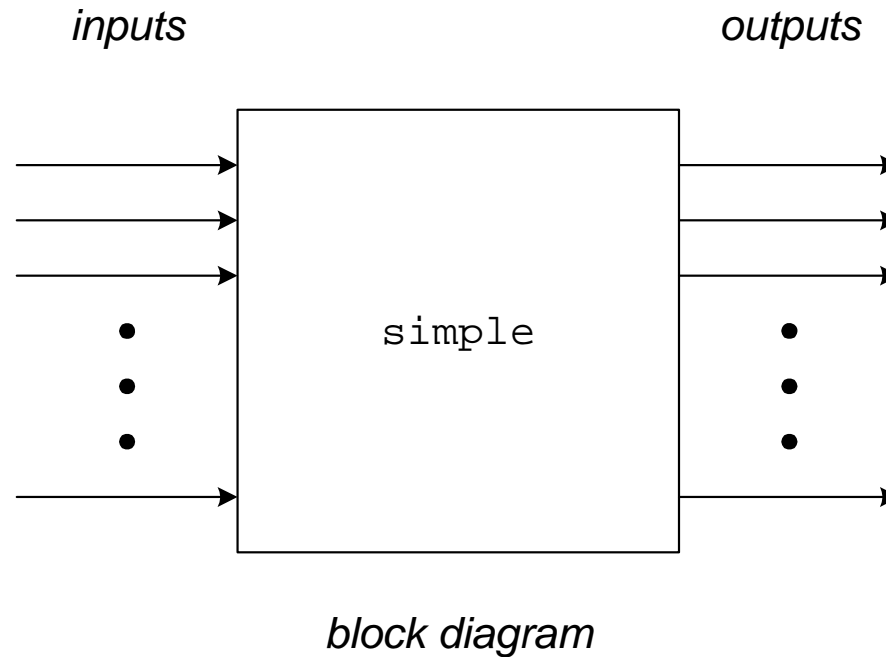

Describes the block diagram of the circuit

- Name of the circuit
- Names & types of the inputs
- Names & types of the outputs

Architecture Body

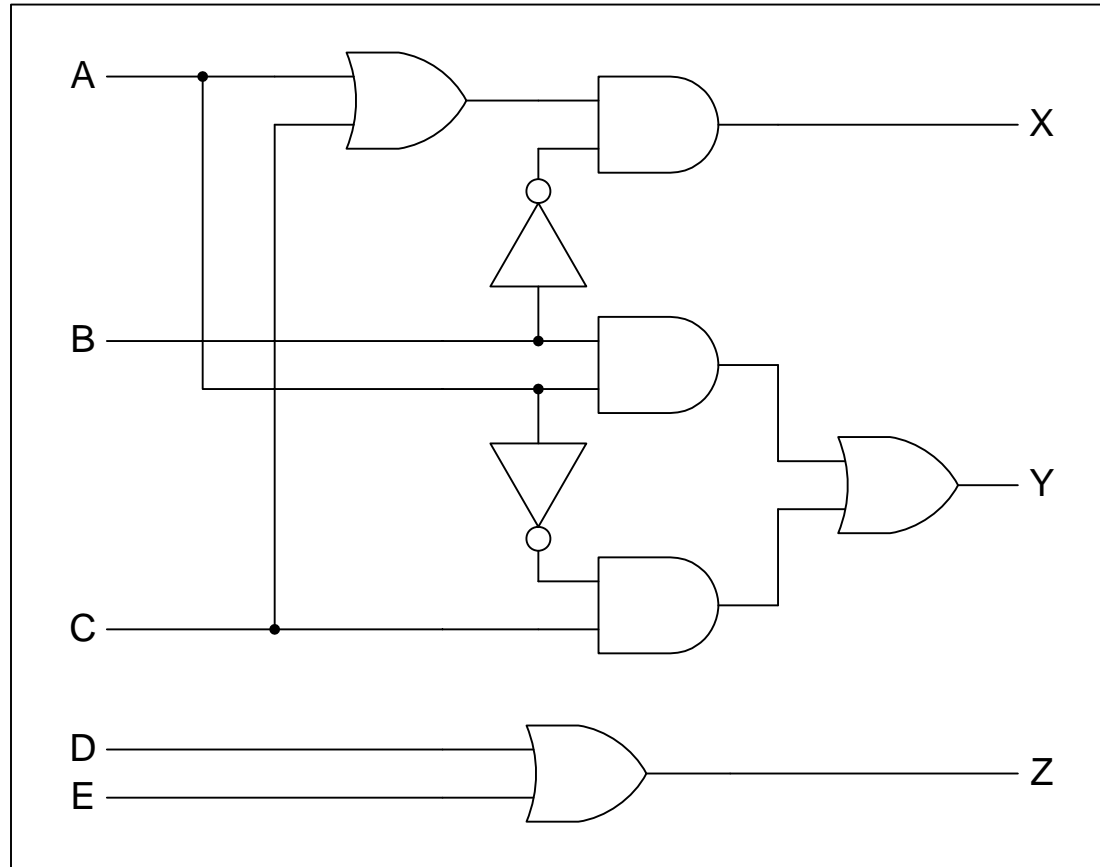

Use statements to describe the circuit functionality


```

ENTITY simple IS
PORT (
    a, b, c, d, e      :IN BIT;
    x, y, z            :OUT BIT);
END simple;


ARCHITECTURE example OF simple IS
BEGIN
    -- signal assignment statements (Boolean)
    x <= (a OR c) AND NOT b;
    y <= (a AND b) OR (NOT a AND c);
    z <= d OR e;
END example;

```

Concurrent vs. Sequential Statements

 

Concurrent

 

Sequential


Concurrent Statements

- execute at same time – in parallel
- order independent
- execute outside of a process

Sequential Statements

- execute one at a time – in sequence
- order dependent
- execute inside a process
- IF, CASE, FOR LOOP

2-input Decoder

 

```
ENTITY decoder2x4 IS
PORT (
    d      :IN BIT_VECTOR (1 DOWNTO 0);
    enable :IN BIT;
    y      :OUT BIT_VECTOR (0 TO 3)
);
END decoder2x4;
```

```


ARCHITECTURE boolean OF decoder2x4 IS
SIGNAL d1bar, d0bar      :BIT;
    -- declare "buried" nodes

BEGIN
    -- write Boolean expressions for outputs
    -- using concurrent signal assignments
y(3) <= NOT (d(1) AND d(0) AND enable);
y(2) <= NOT (d(1) AND d0bar AND enable);
y(1) <= NOT (d1bar AND d(0) AND enable);
y(0) <= NOT (d1bar AND d0bar AND enable);
    -- decoder with active-low outputs
    -- order of statements does not matter
d1bar <= NOT d(1);
d0bar <= NOT d(0);

END boolean;

```

Simulation Results

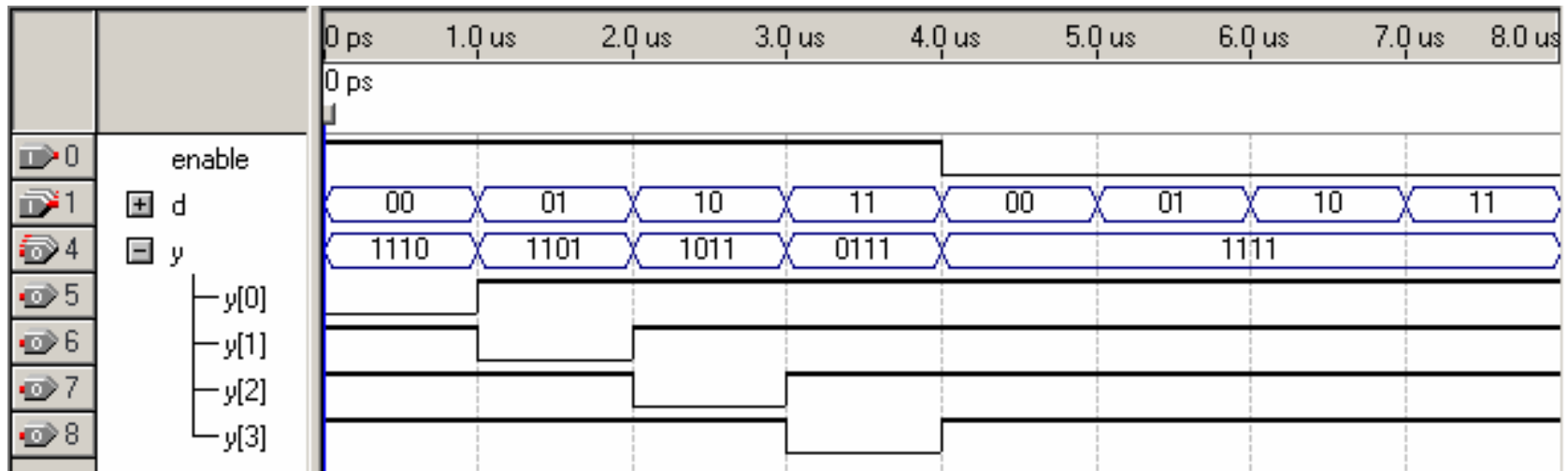

```

ARCHITECTURE conditional OF decoder2x4 IS
BEGIN
-- conditional signal assignment statement
  y <= "0111" WHEN
      (d = "00" AND enable = '1') ELSE

      "1011" WHEN
      (d = "01" AND enable = '1') ELSE

      "1101" WHEN
      (d = "10" AND enable = '1') ELSE

      "1110" WHEN
      (d = "11" AND enable = '1') ELSE

      "1111";
END conditional;

```

```

ARCHITECTURE selected OF decoder2x4 IS
SIGNAL inputs :BIT_VECTOR (2 DOWNTO 0);
    -- define new 3-bit signal array
    -- "buried" within entity
BEGIN
    inputs <= enable & d;
    -- concatenate bits together for new array

    -- selected signal assignment statement
    WITH inputs SELECT
        y <= "0111"  WHEN "100",
            "1011"  WHEN "101",
            "1101"  WHEN "110",
            "1110"  WHEN "111",
            "1111"  WHEN OTHERS;    -- default

END selected;

```

```

ARCHITECTURE behavior OF decoder2x4 IS
BEGIN
PROCESS (d, enable)      -- sensitivity list
-- invoke process if listed inputs change
BEGIN
    IF enable = '1'      THEN
        CASE d IS
            WHEN "00" =>    y <= "0111";
            WHEN "01" =>    y <= "1011";
            WHEN "10" =>    y <= "1101";
            WHEN "11" =>    y <= "1110";
        END CASE;
    ELSE
        y <= "1111";
    END IF;
END PROCESS;
END behavior;

```


Ports

I/O signals in an entity declaration

port declaration → set of ports defined for an entity

each port must have:

name (**identifier**)

direction (**mode**)

[in, out, buffer, inout]

data type

[bit, bit_vector, integer, Boolean,
std_logic, std_logic_vector, enumerated]

Data Types

- every signal must have a data type
- data type defines a set of legal values

Synthesizable Data Types:

BIT	single bit
BIT_VECTOR	array of bits
INTEGER	numerical quantity
<hr/>	
ENUMERATED	define own type
STD_LOGIC	single bit
STD_LOGIC_VECTOR	array of bits

Predefined Standard Data Types

- BOOLEAN (FALSE, TRUE)
- BIT ('0', '1')
- BIT_VECTOR ("0101", "10001101")
- CHARACTER ('A', 'a', 'Z', '5')
- STRING ("Hi!", "Bye")
- INTEGER (345, -1)
- REAL (3.14159, -7.0)
- TIME (10ns, 25ms)

Array

- collection of objects (each one is the same type)
- two standard types: bit vector & string
- do not represent a numerical value
- range is defined when array is declared using “to” or “downto”
- direction of a “slice” of an array must match the direction in which array is declared
- arrays are assigned to each other by matching their position within the array
- single bits and vectors can be concatenated together (using “&” operator)

VHDL Data types

BIT

BIT_VECTOR

INTEGER

ENUMERATED

Example signal assignment statement

```
sig1 <= '1';
```

```
arrayx <= "1011";
```

```
count <= count + 1;
```

```
mytype <= idle;
```

To make an assignment to a signal, the data types on either side of the signal assignment operator must be the same

VHDL Objects

Carry data from place to place in a design

- Signals
 - represent interconnection wires that connect component instantiation ports together
- Variables
 - used for local storage of temporary data
 - visible only inside a process
- Constants
 - used to name specific values
 - can be declared globally, within an architecture, or within a process

Signals

- Like a “wire” inside the circuit (architecture)
- Local signals → visible within the entire architecture
- “Buried” circuit nodes
- Declared before BEGIN
- Can be used in a PROCESS sensitivity list
- Signal assignment operator <=

```
ARCHITECTURE ckt1 OF this_one IS
SIGNAL pets      :BIT;
BEGIN
    pets <= cats AND dogs;
```

Variables

- Local storage of temporary data
- Only declared inside of a PROCESS
- Only visible inside the PROCESS
- Variable assignment operator :=

```
ARCHITECTURE ckt2 OF that_one IS
BEGIN
PROCESS (a, b)
VARIABLE f1          :BIT;
BEGIN
    f1 := NOT a AND b;
```


Process

- Contains sequential statements (IF, CASE)
- Does not execute continuously
- “Invoked” by an “event” on a signal in the “sensitivity list”
- Statements are executed in sequence when a change occurs in a signal in the sensitivity list
- Outputs are “updated” when a process “suspends” at “END PROCESS”
- Multiple processes interact concurrently

Design Units

Smallest item in VHDL that you can compile:

- entity
- architecture
- configuration
- package
- package body
contains body (algorithm) of procedures
or functions for a package

VHDL design file is compiled into a “library” storage area referenced as “work”

Package

contains a collection of definitions that may be referenced by many designs at the same time

- global signals
- constant values
- user defined data types
- component declarations
- subprograms of VHDL code shared between different designs
→ Package Body

```
PACKAGE global_defs IS
    CONSTANT high      :BIT          := '1';
    CONSTANT twelve    :INTEGER      := 12;
    TYPE mytype IS
        (idle, state1, state2, state3, state4);
END global_defs;

USE work.global_defs.ALL;

USE work.global_defs.twelve;

USE work.global_defs.mytype;

-- "work" is the default library for design units
```

Library

Library statement loads library so contents are available when compiling a source file

Use statement makes contents of specified library (packages or other design units) visible to design units in the current source file

If you only use work library, then you just need to specify use statement

```
LIBRARY ieee;
USE IEEE.STD_LOGIC_1164.ALL;

-- to process "standard logic" types, their
-- declarations must be made visible to the
-- entity by way of library and use clauses

ENTITY example IS
PORT (
    a,b    :IN STD_LOGIC;
    c      :IN STD_LOGIC_VECTOR (3 DOWNTO 0);
    z      :OUT STD_LOGIC
);
END example;
```

Standard Logic – IEEE Standard 1164

Defines Multi-Value Logic (MVL)

Provides powerful simulation & debugging tool for designers

U	uninitialized		
X	unknown	}	
0	logic 0	}	strong drive
1	logic 1	}	
Z	high impedance		
W	unknown	}	
L	logic 0	}	weak drive
H	logic 1	}	
-	don't care		

VHDL Operators

Logical	(and or nand nor not xor)
Relational	(< > = <= >= /=)
Arithmetic	(+ - * / ** abs) [integer, real, time data types]


```
entity entity-name is  
    port (list-of-interface-ports);  
end entity-name;  
-- this is a comment line
```

```
architecture architecture-name of entity-name is  
    [architecture-item-declarations]  
begin  
    concurrent-statements:  
        process-statement  
        block-statement  
        concurrent-procedure-call-statement  
        concurrent-assertion-statement  
        concurrent-signal-assignment-statement  
        component-instantiation-statement  
        generate-statement  
end architecture-name ;
```

[process-label:] **process** [*(sensitivity-list)*] [**is**]
 [process-item-declarations]
begin
 sequential-statements:
 variable-assignment-statement
 signal-assignment-statement
 wait-statement
 if-statement
 case-statement
 loop-statement
 null-statement
 exit-statement
 next-statement
 assertion-statement
 report-statement
 procedure-call-statement
 return-statement
end process [*process-label*] ;

```

    -- 2-channel multiplexer
ENTITY mux2to1 IS
PORT (a, b      :IN BIT;
      s        :IN BIT;
      y        :OUT BIT);
END mux2to1;

ARCHITECTURE ex1 OF mux2to1 IS
BEGIN
    y <= a WHEN s = '0' ELSE b;
    -- conditional signal assignment
END ex1;

```

```

ARCHITECTURE ex2 OF mux2to1 IS
BEGIN
PROCESS (a, b, s)
BEGIN
    IF s = '0' THEN y <= a; -- IF statement
    ELSE y <= b;
    END IF;
END PROCESS;
END ex2;

-- 2-channel, 4-bit multiplexer
ENTITY mux2to1 IS
PORT (a, b :IN BIT_VECTOR (3 DOWNTO 0);
      s :IN BIT;
      y :OUT BIT_VECTOR (3 DOWNTO 0));
END mux2to1;


```

```

ENTITY mux4to1 IS      -- 4-channel, 4-bit MUX
PORT (a, b             :IN BIT_VECTOR (3 DOWNTO 0);
      c, d             :IN BIT_VECTOR (3 DOWNTO 0);
      s               :IN BIT_VECTOR (1 DOWNTO 0);
      y               :OUT BIT_VECTOR (3 DOWNTO 0));
END mux4to1;
ARCHITECTURE ex3 OF mux4to1 IS
BEGIN
PROCESS (a, b, c, d, s)
BEGIN
    CASE s IS
        WHEN "00"      =>    y <= a;
        WHEN "01"      =>    y <= b;
        WHEN "10"      =>    y <= c;
        WHEN "11"      =>    y <= d;
    END CASE;
END PROCESS;
END ex3;

```

4-channel, 4-bit MUX Simulation

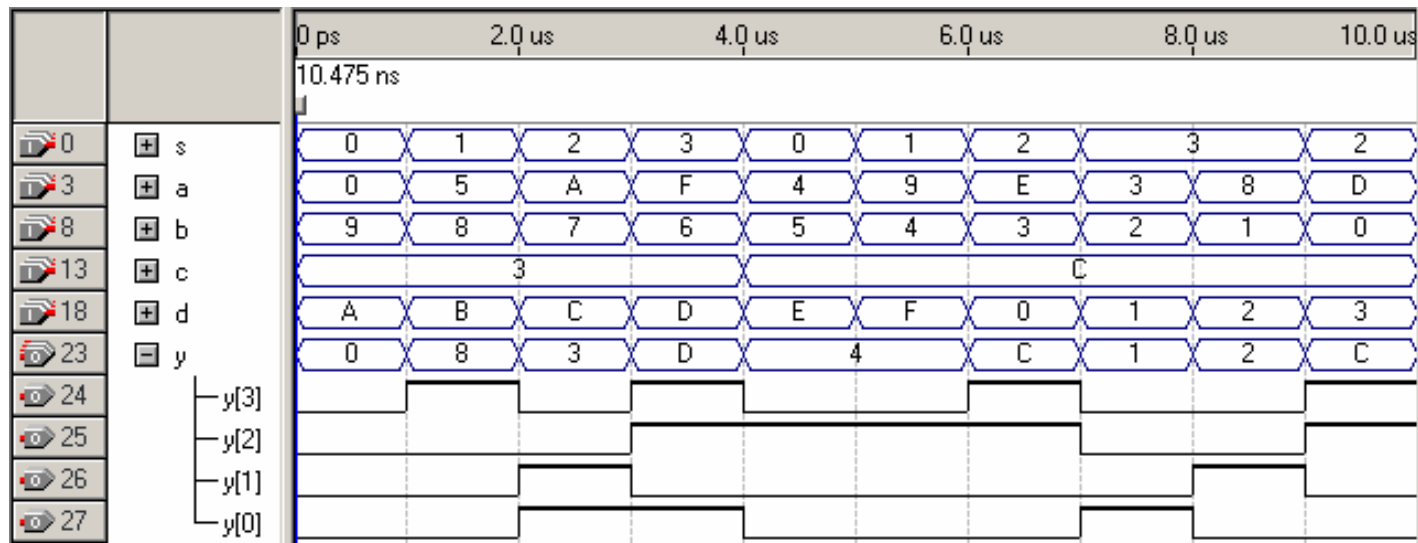

```

    -- transparent latch
ENTITY d_latch IS
PORT (d, enable      :IN BIT;
      q              :OUT BIT);
END d_latch;

ARCHITECTURE level_enabled OF d_latch IS
BEGIN
PROCESS (d, enable)
BEGIN
    -- enabled with high logic level
    IF enable = '1' THEN q <= d;
    END IF;
    -- memory is implied, no else statement
END PROCESS;
END level_enabled;

```


```

    -- clocked D flip-flop
ENTITY dflipflop IS
PORT (d, clock      :IN BIT;
      q             :OUT BIT);
END dflipflop;


ARCHITECTURE edge_triggered OF dflipflop IS
BEGIN
PROCESS (clock)
BEGIN
    -- triggers on rising edge
    IF (clock = '1' AND clock'EVENT) THEN
        q <= d;
    END IF;
    -- 'EVENT signal attribute
END PROCESS;
END edge_triggered;

```


Transparent D Latch Simulation

 

Clocked D Flip-flop Simulation

 

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
                                -- using Standard Logic

ENTITY dflipflop IS
PORT (d, clock      :IN  STD_LOGIC;
      q              :OUT STD_LOGIC);
END dflipflop;
ARCHITECTURE edge_trig OF dflipflop IS
BEGIN
PROCESS (clock)
BEGIN
IF (RISING_EDGE(clock)) THEN    q <= d;
    -- also FALLING_EDGE() detection
END IF;
END PROCESS;
END edge_trig;

```

```

ENTITY d_ff IS
PORT (data, clock, preset, clear :IN BIT;
      q_out :OUT BIT);
END d_ff;

ARCHITECTURE asynchronous OF d_ff IS
BEGIN
PROCESS (clock, preset, clear)
BEGIN
    -- priority order: clear, preset, clock
    IF (clear = '0') THEN q_out <= '0';
    ELSIF (preset = '0') THEN q_out <= '1';
    ELSIF (clock'EVENT AND clock = '0') THEN
        q_out <= data;
    END IF;
END PROCESS;
END asynchronous;

```

```

    -- mod-16 up/down binary counter
ENTITY updnctr IS
PORT (
    clock, dir    :IN BIT;
    q              :OUT INTEGER RANGE 0 TO 15
        -- output q will need 4 bits
);
END updnctr;

ARCHITECTURE binary OF updnctr IS
BEGIN

PROCESS (clock)    -- clock change?

    VARIABLE count    :INTEGER RANGE 0 TO 15;
    -- create a variable for counter value

```

```


BEGIN
  IF (clock'EVENT AND clock = '1') THEN
    IF (dir = '1') THEN -- count up
      count := count + 1;
    ELSE -- count down
      count := count - 1;
    END IF;
  END IF; -- count holds with no clock

  q <= count;
  -- send count value to output port

END PROCESS;
END binary;

```

Mod-16 Up/Down Binary Counter Simulation

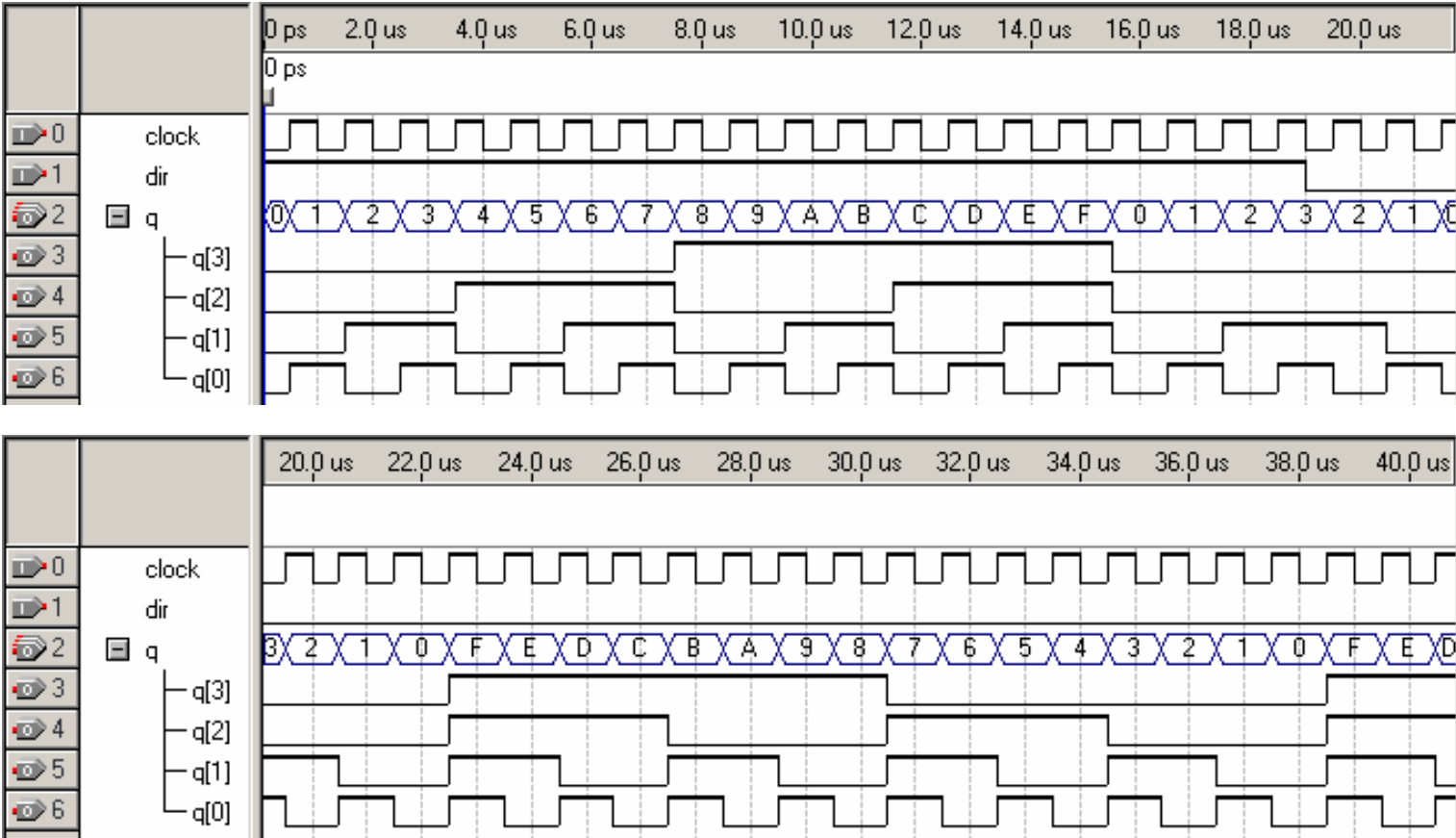

```

ENTITY mod10 IS
PORT (
    clock, enable      :IN BIT;
    load, clear        :IN BIT;
    d                  :IN INTEGER RANGE 0 TO 15;
    q                  :OUT INTEGER RANGE 0 TO 15;
    rco                :OUT BIT
);
END mod10;

ARCHITECTURE bcd OF mod10 IS
BEGIN
PROCESS (clock, clear, enable)
    -- asynchronous clear
    VARIABLE counter :INTEGER RANGE 0 TO 15;

BEGIN

```

```

IF (clear = '1') THEN      counter := 0;
    -- asynchronous clear has priority

ELSIF (clock'EVENT AND clock = '1') THEN

    IF (load = '1') THEN  counter := d;
        -- synchronous load

    ELSIF (enable = '1') THEN

        IF (counter = 9) THEN      -- recycle
            counter := 0;
        ELSE
            counter := counter + 1;
        END IF;
        -- hold count behavior is implied
    END IF;
END IF;

```



```
-- rco detects terminal count when enabled
IF ((counter = 9) AND (enable = '1')) THEN
    rco <= '1';
ELSE
    rco <= '0';
END IF;

q <= counter; -- output counter to ports

END PROCESS;
END bcd;
```

