 


“Simple”



```


ENTITY simple IS
PORT (
    a, b, c, d, e           :IN BIT;
    x, y, z                 :OUT BIT);
END simple;

```

```

ARCHITECTURE example OF simple IS
BEGIN
    -- signal assignment statements (Boolean)
    x <= (a OR c) AND NOT b;
    y <= (a AND b) OR (NOT a AND c);
    z <= d OR e;
END example;

```

 

```

ENTITY decoder2x4 IS
PORT (
    d      :IN BIT_VECTOR (1 DOWNTO 0);
    enable  :IN BIT;
    y      :OUT BIT_VECTOR (0 TO 3)
);
END decoder2x4;

```

```


ARCHITECTURE boolean OF decoder2x4 IS
    SIGNAL d1bar, d0bar      :BIT;      -- declare "buried" nodes

BEGIN
    -- write Boolean expressions for outputs
    -- using concurrent signal assignments
    y(3) <= NOT (d(1) AND d(0) AND enable);
    y(2) <= NOT (d(1) AND d0bar AND enable);
    y(1) <= NOT (d1bar AND d(0) AND enable);
    y(0) <= NOT (d1bar AND d0bar AND enable);
    -- decoder with active-low outputs
    -- order of statements does not matter
    d1bar <= NOT d(1);
    d0bar <= NOT d(0);

END boolean;

```

Simulation Results

 

```

ARCHITECTURE conditional OF decoder2x4 IS
BEGIN
-- conditional signal assignment statement
    y <= "0111"    WHEN (d = "00" AND enable = '1') ELSE
        "1011"    WHEN (d = "01" AND enable = '1') ELSE
        "1101"    WHEN (d = "10" AND enable = '1') ELSE
        "1110"    WHEN (d = "11" AND enable = '1') ELSE
        "1111";
END conditional;

```

```

ARCHITECTURE selected OF decoder2x4 IS
SIGNAL    inputs    :BIT_VECTOR (2 DOWNTO 0);
-- define new 3-bit signal array "buried" within entity
BEGIN
    inputs <= enable & d;
-- concatenate bits together for new array
-- selected signal assignment statement
    WITH inputs SELECT
        y <= "0111"    WHEN "100",
            "1011"    WHEN "101",
            "1101"    WHEN "110",
            "1110"    WHEN "111",
            "1111"    WHEN OTHERS;           -- default
END selected;

```

```

ARCHITECTURE behavior OF decoder2x4 IS
BEGIN
PROCESS (d, enable)
-- sensitivity list, invoke process if listed inputs change
BEGIN
    IF enable = '1'    THEN
        CASE d IS
            WHEN "00" =>        y <= "0111";
            WHEN "01" =>        y <= "1011";
            WHEN "10" =>        y <= "1101";
            WHEN "11" =>        y <= "1110";
        END CASE;
    ELSE
        y <= "1111";
    END IF;
END PROCESS;
END behavior;

```

```

entity entity-name is
    port (list-of-interface-ports);
end entity-name;
-- this is a comment line

architecture architecture-name of entity-name is
    [architecture-item-declarations]
begin
    concurrent-statements:
        process-statement
        block-statement
        concurrent-procedure-call-statement
        concurrent-assertion-statement
        concurrent-signal-assignment-statement
        component-instantiation-statement
        generate-statement
end architecture-name ;

```

```

[process-label:] process [(sensitivity-list)] [is]
    [process-item-declarations]
begin
    sequential-statements:
        variable-assignment-statement
        signal-assignment-statement
        wait-statement
        if-statement
        case-statement
        loop-statement
        null-statement
        exit-statement
        next-statement
        assertion-statement
        report-statement
        procedure-call-statement
        return-statement
end process [process-label] ;

```

```

    -- 2-channel multiplexer
ENTITY mux2to1 IS
PORT (a, b      :IN BIT;
      s         :IN BIT;
      y         :OUT BIT);
END mux2to1;

ARCHITECTURE ex1 OF mux2to1 IS
BEGIN
    y <= a WHEN s = '0' ELSE b;
    -- conditional signal assignment
END ex1;

```

```

ARCHITECTURE ex2 OF mux2to1 IS
BEGIN
PROCESS (a, b, s)
BEGIN
    IF s = '0'      THEN y <= a;          -- IF statement
    ELSE           y <= b;
    END IF;
END PROCESS;
END ex2;

```

```

    -- 2-channel, 4-bit multiplexer
ENTITY mux2to1 IS
PORT (a, b      :IN BIT_VECTOR (3 DOWNT0 0);
      s         :IN BIT;
      y         :OUT BIT_VECTOR (3 DOWNT0 0));
END mux2to1;

```

```

ENTITY mux4to1 IS          -- 4-channel, 4-bit MUX
PORT (a, b                 :IN BIT_VECTOR (3 DOWNTO 0);
      c, d                 :IN BIT_VECTOR (3 DOWNTO 0);
      s                   :IN BIT_VECTOR (1 DOWNTO 0);
      y                   :OUT BIT_VECTOR (3 DOWNTO 0));
END mux4to1;

```

```

ARCHITECTURE ex3 OF mux4to1 IS

```

```

BEGIN

```

```

PROCESS (a, b, c, d, s)

```

```

BEGIN

```

```

    CASE s IS

```

```

        WHEN "00"      =>      y <= a;

```

```

        WHEN "01"      =>      y <= b;

```

```

        WHEN "10"      =>      y <= c;

```

```

        WHEN "11"      =>      y <= d;

```

```

    END CASE;

```

```

END PROCESS;


```

```

END ex3;

```

4-channel, 4-bit MUX Simulation

 

```

    -- transparent latch
ENTITY d_latch IS
PORT (d, enable      :IN BIT;
      q              :OUT BIT);
END d_latch;
ARCHITECTURE level_enabled OF d_latch IS
BEGIN
PROCESS (d, enable)
BEGIN
    -- enabled with high logic level
    IF enable = '1' THEN q <= d;
    END IF;
    -- memory is implied, no else statement
END PROCESS;
END level_enabled;


```

```


    -- clocked D flip-flop
ENTITY dflipflop IS
PORT (d, clock       :IN BIT;
      q              :OUT BIT);
END dflipflop;
ARCHITECTURE edge_triggered OF dflipflop IS
BEGIN
PROCESS (clock)
BEGIN
    -- triggers on rising edge
    IF (clock = '1' AND clock'EVENT) THEN q <= d;
    END IF;
    -- 'EVENT signal attribute
END PROCESS;
END edge_triggered;

```

Transparent D Latch Simulation

 

Clocked D Flip-flop Simulation

 

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
    -- using Standard Logic

ENTITY dflipflop IS
PORT (d, clock      :IN STD_LOGIC;
      q             :OUT STD_LOGIC);
END dflipflop;

ARCHITECTURE edge_trig OF dflipflop IS
BEGIN
PROCESS (clock)
BEGIN
IF (RISING_EDGE(clock)) THEN      q <= d;
    -- also FALLING_EDGE() detection
END IF;
END PROCESS;
END edge_trig;

```

```

ENTITY d_ff IS
PORT (data, clock, preset, clear  :IN BIT;
      q_out                      :OUT BIT);
END d_ff;

ARCHITECTURE asynchronous OF d_ff IS
BEGIN
PROCESS (clock, preset, clear)
BEGIN
    -- priority order: clear, preset, clock
    IF (clear = '0') THEN      q_out <= '0';
    ELSIF (preset = '0') THEN  q_out <= '1';
    ELSIF (clock'EVENT AND clock = '0') THEN
                                q_out <= data;
    END IF;
END PROCESS;
END asynchronous;

```


```

    -- mod-16 up/down binary counter
ENTITY updnctr IS
PORT (
    clock, dir      :IN BIT;
    q               :OUT INTEGER RANGE 0 TO 15
    -- output q will need 4 bits
);
END updnctr;

ARCHITECTURE binary OF updnctr IS
BEGIN
PROCESS (clock)      -- clock change?
    VARIABLE count    :INTEGER RANGE 0 TO 15;
    -- create a variable for counter value
BEGIN
    IF (clock'EVENT AND clock = '1') THEN
        IF (dir = '1') THEN    -- count up
            count := count + 1;
        ELSE                   -- count down
            count := count - 1;
        END IF;
    END IF;
    -- count holds with no clock
    q <= count;               -- send count value to output port
END PROCESS;
END binary;

```

Mod-16 Up/Down Binary Counter Simulation

 

```

ENTITY mod10 IS
PORT (
    clock, enable      :IN BIT;
    load, clear        :IN BIT;
    d                  :IN INTEGER RANGE 0 TO 15;
    q                  :OUT INTEGER RANGE 0 TO 15;
    rco                :OUT BIT
);
END mod10;

ARCHITECTURE bcd OF mod10 IS
BEGIN

PROCESS (clock, clear, enable)    -- asynchronous clear
    VARIABLE counter      :INTEGER RANGE 0 TO 15;
BEGIN
    IF (clear = '1') THEN          counter := 0;
        -- asynchronous clear has priority
    ELSIF (clock'EVENT AND clock = '1') THEN
        IF (load = '1') THEN      counter := d;
            -- synchronous load
        ELSIF (enable = '1') THEN
            IF (counter = 9) THEN  -- recycle
                counter := 0;
            ELSE
                counter := counter + 1;
            END IF;
            -- hold count behavior is implied
        END IF;
    END IF;

    -- rco detects terminal count when enabled
    IF ((counter = 9) AND (enable = '1')) THEN
        rco <= '1';
    ELSE
        rco <= '0';
    END IF;

    q <= counter;                  -- output counter to ports
END PROCESS;
END bcd;

```

BCD Counter Simulation

